

GF2 Software - Second Interim Report

Jonty Page
Pembroke College, University of Cambridge

May 30, 2019

1 Example Definition Files and Circuits

1.1 Example 1 - Full Adder Circuit

1.1.1 Full Adder Circuit Diagram

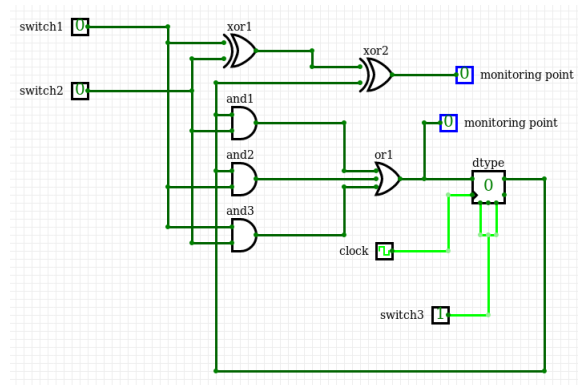


Figure 1: Full Adder Circuit Diagram

1.1.2 Full Adder Circuit Definition File

```
DEVICES {  
switch1: SWITCH, initial 0;  
switch2: SWITCH, initial 0;  
switch3: SWITCH, initial 0;  
xor1: XOR;  
xor2: XOR;  
and1: AND, inputs 2;  
and2: AND, inputs 2;  
and3: AND, inputs 2;  
or1: OR, inputs 3;  
clock: CLOCK, period 5;  
dtype: DTYPE;  
}
```

```
CONNECT {  
switch1 = xor1.I1;  
switch1 = and2.I2;  
switch1 = and3.I1;  
switch2 = and1.I2;  
switch2 = xor1.I2;  
switch2 = and3.I2;  
clock = dtype.CLK;  
}
```

```

xor1 = xor2.I1;
and1 = or1.I1;
and2 = or1.I2;
and3 = or1.I3;
or1 = dtype.DATA;
switch3 = dtype.SET;
switch3 = dtype.CLEAR;
dtype.Q = xor2.I2;
dtype.Q = and1.I1;
dtype.Q = and2.I1;
}

```

```

MONITOR{
xor2;
or1;
}
END

```

1.2 Example 2 - Shift Register

1.2.1 Shift Register Circuit Diagram

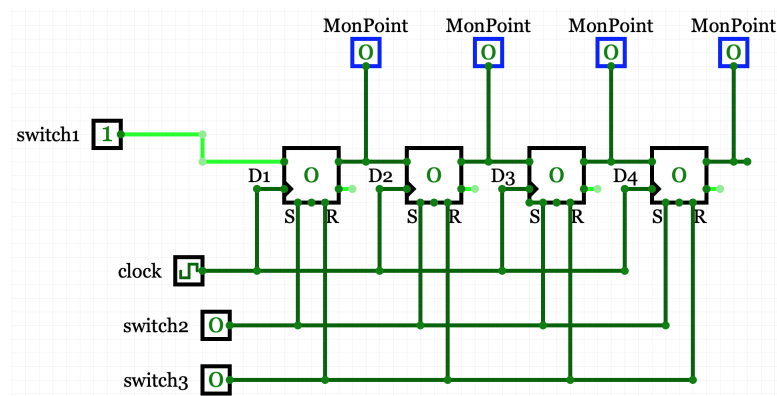


Figure 2: Shift Register Circuit Diagram

1.2.2 Shift Register Circuit Definition File

```

DEVICES{
switch1: SWITCH, initial 1;
switch2: SWITCH, initial 0;
switch3: SWITCH, initial 0;
D1: DTYPE;
D2: DTYPE;
D3: DTYPE;
D4: DTYPE;
clock: CLOCK, period 5;
}

CONNECT{
switch1 = D1.DATA;
D1.Q = D2.DATA;
D2.Q = D3.DATA;
D3.Q = D4.DATA;
clock = D1.CLK;
clock = D2.CLK;
}

```

```

clock = D3.CLK;
clock = D4.CLK;
switch2 = D1.SET;
switch2 = D2.SET;
switch2 = D3.SET;
switch2 = D4.SET;
switch3 = D1.CLEAR;
switch3 = D2.CLEAR;
switch3 = D3.CLEAR;
switch3 = D4.CLEAR;
}

```

```

MONITOR{
D1.Q;
D2.Q;
D3.Q;
D4.Q;
}

```

```

END

```

1.3 Example 3 - Combinational Circuit

1.3.1 Combinational Circuit Diagram

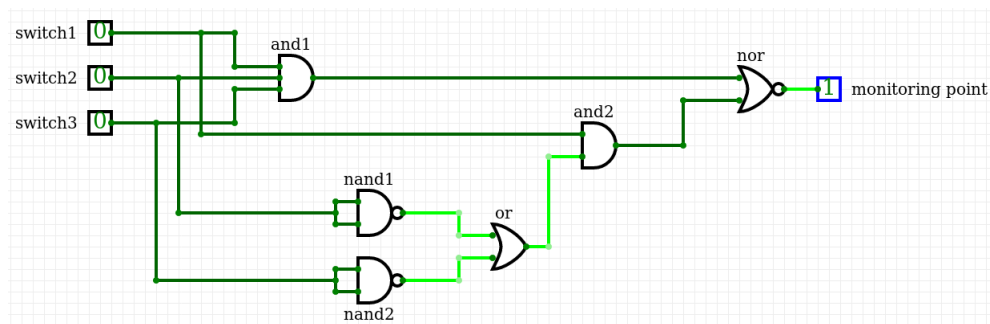


Figure 3: Shift Register Circuit Diagram

1.3.2 Combinational Circuit Definition File

```

DEVICES{
switch1: SWITCH, initial 0;
switch2: SWITCH, initial 0;
switch3: SWITCH, initial 0;
and1: AND, inputs 3;
and2: AND, inputs 2;
nand1: NAND, inputs 2;
nand2: NAND, inputs 2;
or: OR, inputs 2;
nor: NOR, inputs 2;
}

```

```

CONNECT{
switch1 = and1.I1;
switch1 = and2.I1;
switch2 = and1.I2;
switch2 = nand1.I1;

```

```
MONITOR{
nor;
}
```

END

1.4 Example 4 - dtype Circuit

1.4.1 dtype Circuit Diagram

 


Figure 4: dtype Circuit Diagram

1.4.2 dtype Circuit Definition File

```
DEVICES{
switch: SWITCH, initial 0;
clock: CLOCK, period 5;
nand1: NAND, inputs 2;
nand2: NAND, inputs 2;
nand3: NAND, inputs 2;
nand4: NAND, inputs 2;
nand5: NAND, inputs 2;
}
```

```
CONNECT{
clock = nand2.I2;
clock = nand1.I2;
switch = nand1.I1;
switch = nand5.I1;
switch = nand5.I2;
nand5 = nand2.I1;
nand1 = nand3.I1;
nand2 = nand4.I2;
nand3 = nand4.I1;
nand4 = nand3.I2;
}
```

```
MONITOR{  
nand3;  
nand4;  
}  
END
```